
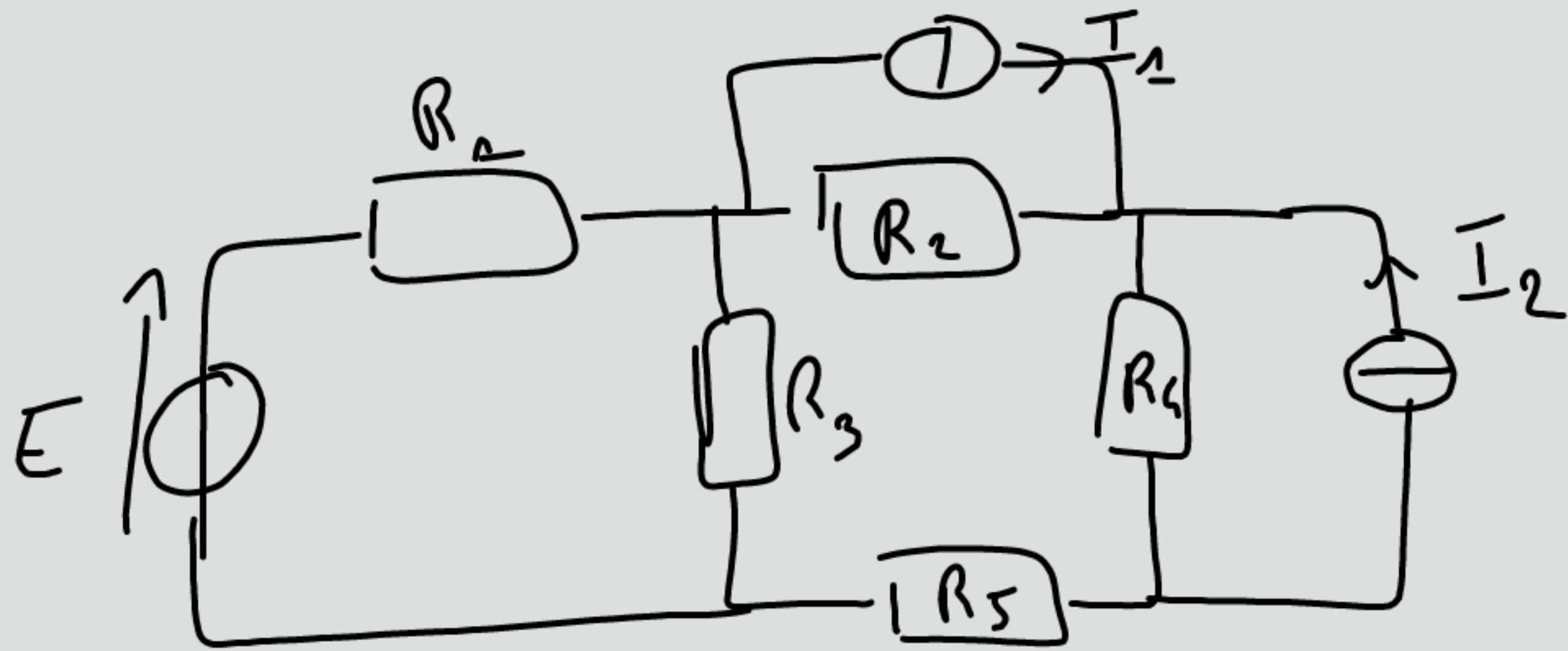


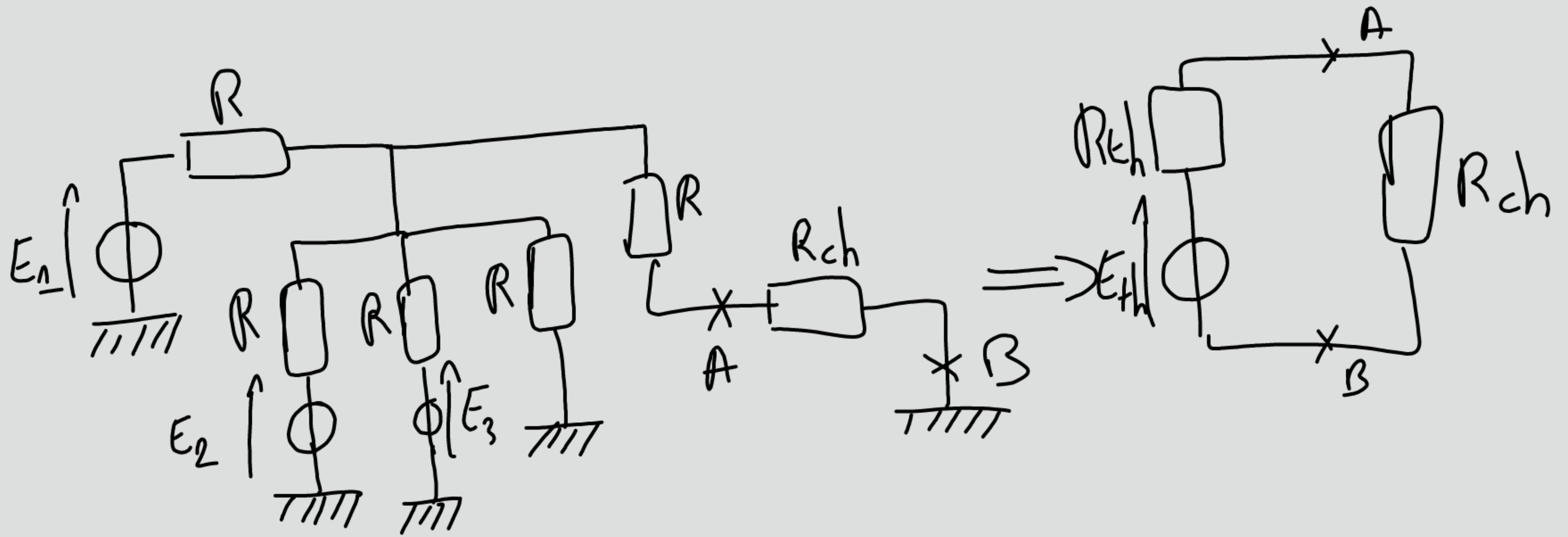


$$P = U \times I$$

$$P = R I^2$$


$$(a+b)^2 \neq a^2 + b^2$$



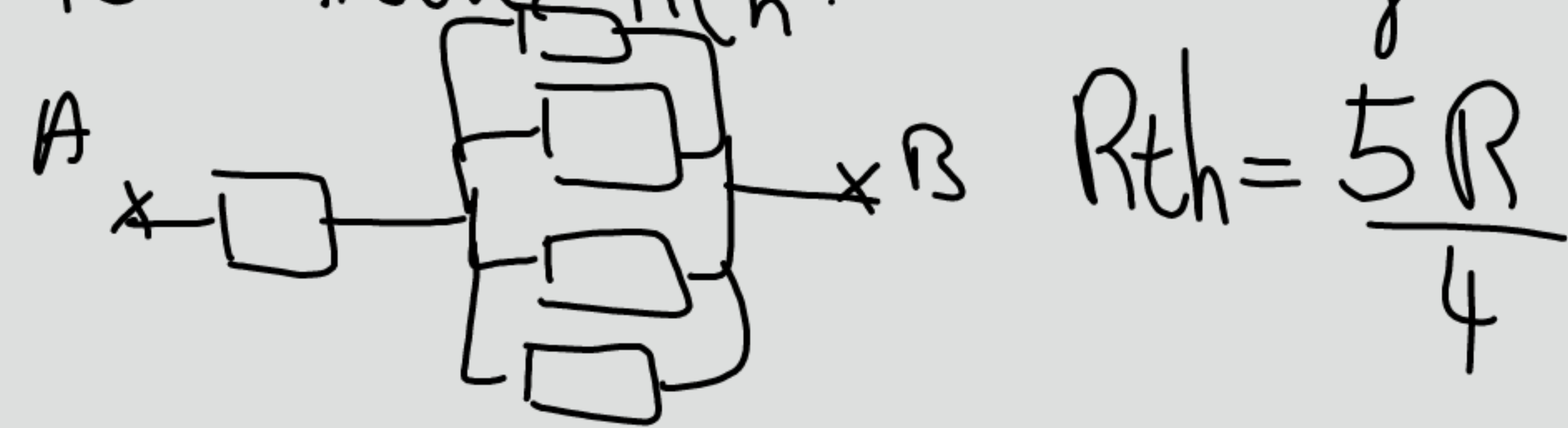Pour trouver R_{th} : on éteint les géné et on calcule $R_{eq} = R_{th}$.




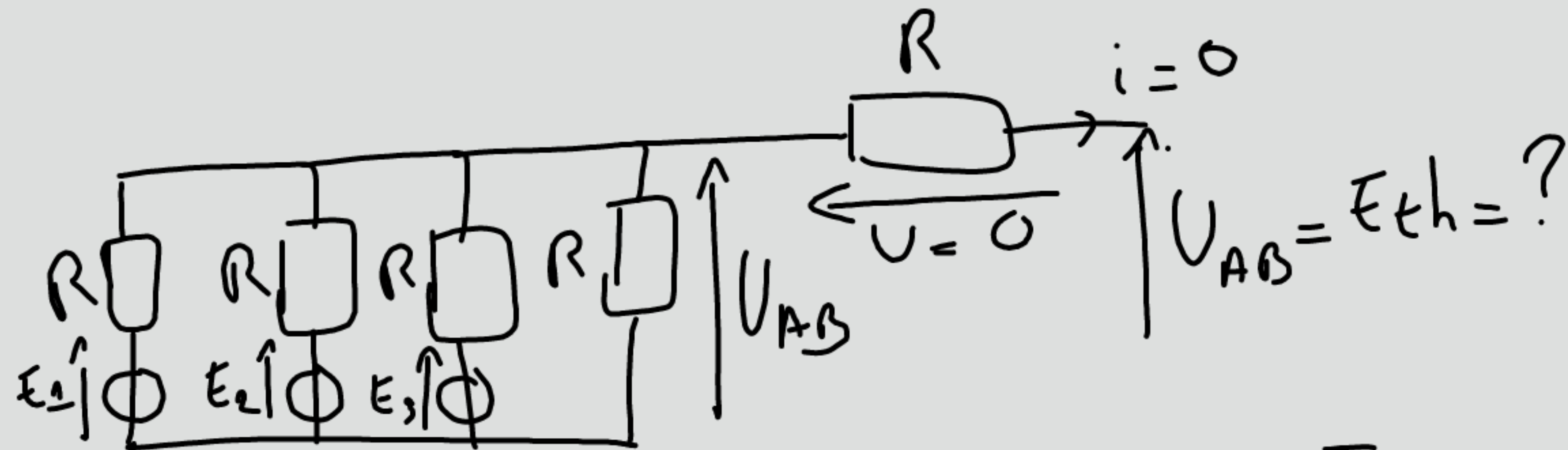Pour trouver E_{th} , on met un circuit ouvert entre A et B:



D'après Millman,
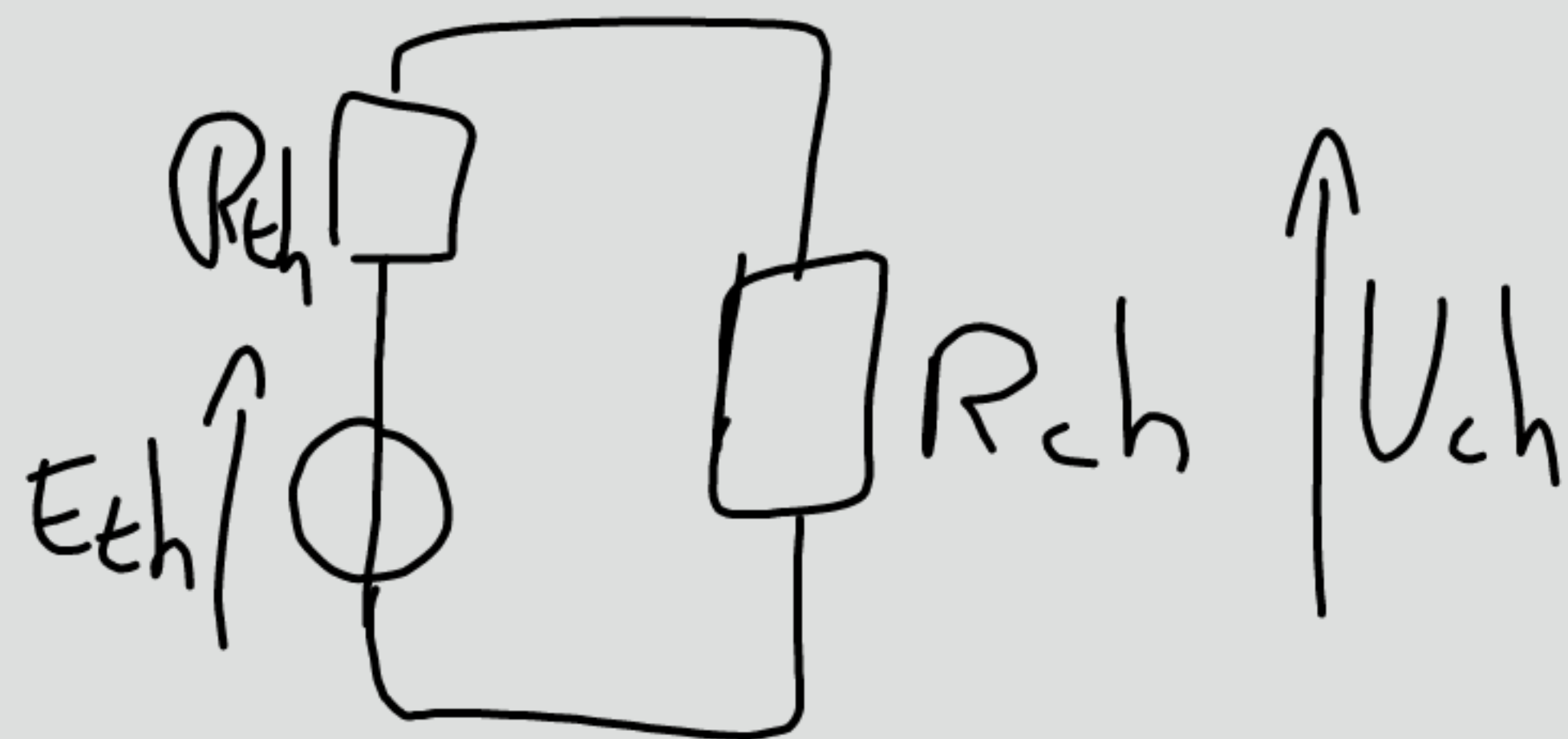
$$V_{AB} = \frac{\sum_i \frac{E_i}{R_i}}{\sum_i \frac{1}{R_i}} = \frac{\frac{E_1}{R} + \frac{E_2}{R} + \frac{E_3}{R} + \frac{0}{R}}{\frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{R}} = \frac{(E_1 + E_2 + E_3)}{4} = E_{th}$$




Diviseur de tension:

$$V_{ch} = \frac{R_{ch}}{R_{ch} + R_{th}} \times E_{th} = \frac{R}{R + \frac{5R}{4}} \times \frac{(E_1 + E_2 + E_3)}{4} = \frac{4}{9} \times \frac{E_1 + E_2 + E_3}{4} = \frac{E_1 + E_2 + E_3}{9}$$

TD 3

Exercice 1:

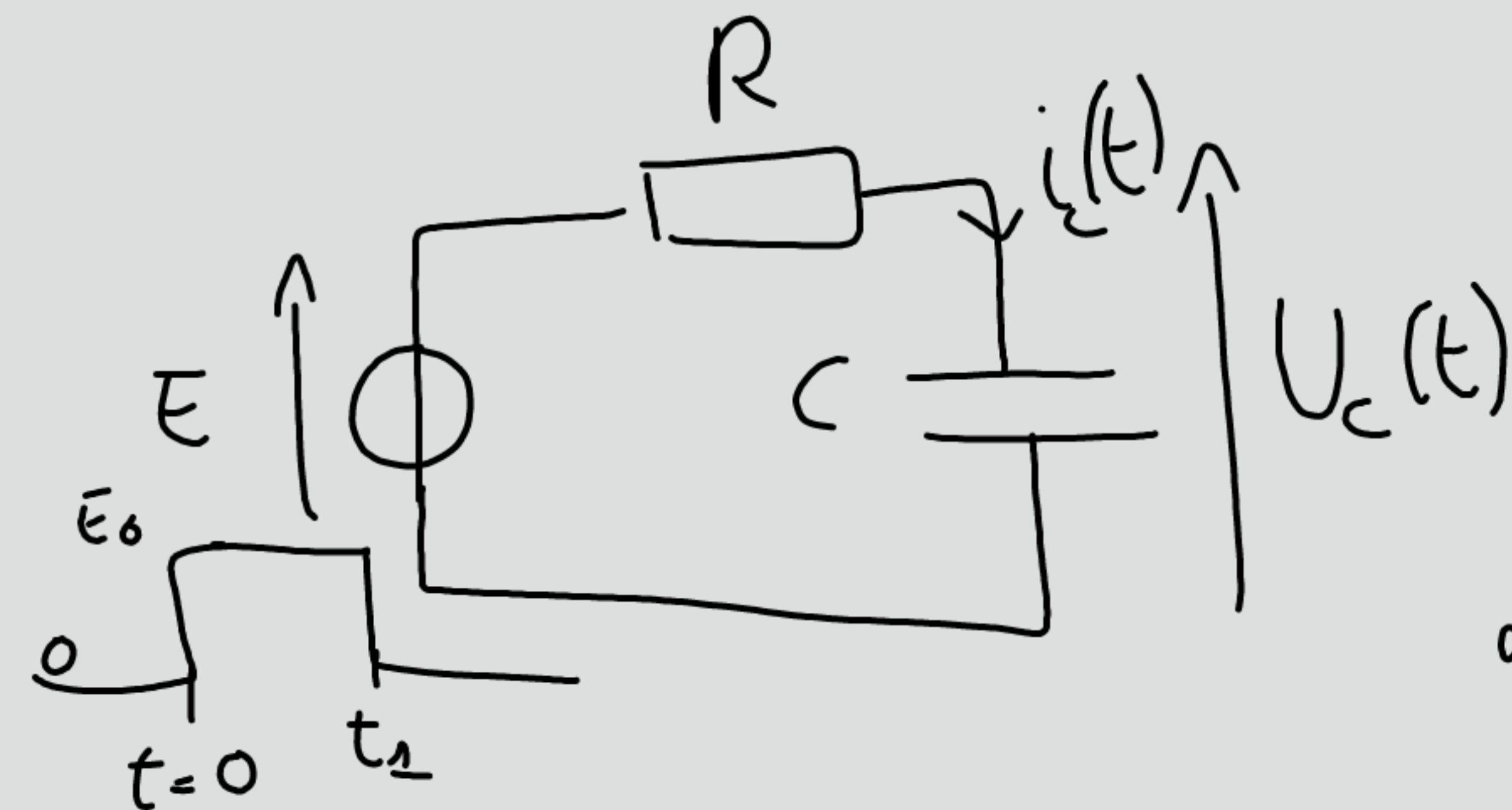

Loi des mailles:

$$E = U_R + U_C$$

$$E = Ri + U_C$$

$$E = RC \frac{dU_C}{dt} + U_C$$

La solution est de la forme

$$U_C(t) = Ae^{-t/RC} + B$$

Conditions aux limites:

$$A' \ t=0 \quad U_c(t)=0 \quad \text{par lecture du circuit}$$

$$U_c(t) = Ae^{-t/RC} + B = A+B \quad \text{par la forme de la solution}$$

$$\therefore \Rightarrow 0 = A+B \Rightarrow A = -B$$

$$A' \ t \rightarrow \infty \quad U_c(\infty) = E_0 \quad \text{par lecture du circuit}$$

$$U_c(\infty) = B \quad \text{par la forme de la solution}$$

$$\text{Finalement, } U_c(t) = -E_0 e^{-t/RC} + E_0 = E_0(1 - e^{-t/RC})$$

$$V = E - U_c(t)$$

$$V = E_0 - E_0(1 - e^{-t/RC})$$

$$V(t) = E_0 e^{-t/RC}$$

$$\tau = RC = 1k \times 1\mu = 1ms$$

$$t_1 = 50ms \gg \tau$$

$$t_2 = 2ms$$



